

2-way Doherty amplifier with BLF888A Rev. 2 — 1 September 2015

Application note

Document information

Info	Content
Keywords	BLF888A, Doherty, DVB-T, UHF
Abstract	This document gives a description and measurement results of a 2-way Doherty amplifier using $2 \times BLF888A$ UHF LDMOS transistors.

Revision history

Rev	Date	Description
v.2	20150901	Modifications
		 The format of this document has been redesigned to comply with the new identity guidelines of Ampleon.
		 Legal texts have been adapted to the new company name where appropriate.
v.1	20131114	Initial version

Contact information

For more information, please visit: http://www.ampleon.com

For sales office addresses, please visit: http://www.ampleon.com/sales

AN11325#2

Application note

1. Introduction

The document introduces a narrowband 2-way Doherty amplifier (test) demo board. Using the board together with modeling software and measuring test equipment, details of amplifier designs for three DBV-T frequencies are given. The process of the designs and the measurements and modeling results are also given.

The test board comprises one PCB containing the broadband main and peaking amplifiers, and a second PCB containing the Doherty combiner. The main and peaking amplifiers each uses a BLF888A UHF LDMOS transistor, together with associated components. The broadband amplifier blocks cover the whole UHF band.

Amplifier bandwidth and base frequency is dependent on the Doherty combiner design. Several narrowband design versions of the Doherty combiner PCB can be built and interchanged on the demo board to determine the required amplifier frequency.

The amplifier has minimum output power of 200 W average (DBV-T) and approximately 50 MHz of bandwidth (depending on the center frequency).



Further details of the demo board operating conditions can be found at Section 6.

2. Test circuit

The test board contains two broadband BLF888A amplifiers on one common PCB (for main and peaking). The electrical circuit is completed with a Doherty combiner on a separate PCB. This combiner PCB can be replaced by another unit when changing to another frequency. The bandwidth of the Doherty amplifier is limited to approximately

AN11325#2

All information provided in this document is subject to legal disclaimers.

50 MHz. The broadband 50 Ω amplifiers cover the whole UHF band and are not further optimized for Doherty operation. An advantage is that only the Doherty combiner needs to be redesigned per frequency band. The disadvantage is the lower efficiency compared to a narrow band design of the amplifier blocks.

The main amplifier operates in class AB and the peaking amplifier operates in class C.

The Doherty combiner consists of two offset lines (main/peaking) and a 90° transmission line (impedance inverter). The matching to 50 Ω is achieved by the addition of a 35 Ω transmission line (25 Ω to 50 Ω). This is less critical in design. Section 3 discusses the combiner offset lines.

3. Measurement and modeling

The characteristics of the offset lines were determined by measurement and modeling.

3.1 Measurement with Network Analyzer

By the use of test structures (<u>Figure 2</u> and <u>Figure 3</u>), offset lines were measured using a network analyzer for S11 as a function of frequency (see Figure 4).

The test structures can be put on the module instead of the separate Doherty combiner PCB. By putting the supply voltage on the peaking amplifier only and choosing the right length on the PCB, the offset line can be measured. The length can be chosen by soldering the links on the PCB.

Connect the peaking amplifier and select a length on the test structure. The center frequency of the offset line is then the point where the impedance is infinite on the Smith chart (Figure 4).



© Ampleon The Netherlands B.V. 2015. All rights reserved

2-way Doherty amplifier with BLF888A



- The same offset lines were used for both Main and Peaking amplifier.
- The ideal offset line of the peaking amplifier is open at the combiner point (see Figure 4).
- Pulsed measurement (efficiency) at back-off power showed that this was also correct for the main amplifier.

3.2 Modeling

The characteristics of the offset line can be determined by passive models (equivalent), or active models of the transistor. Both methods give similar results. Figure 5 shows the broadband (peaking) amplifier output matching (block X5, BB_output_888A) and the active models (component X2 and X7). Figure 6 shows the broadband matching configuration of BLF888A in detail.

2-way Doherty amplifier with BLF888A



AMPLEON

2-way Doherty amplifier with BLF888A

AN11325



3.3 Measurement results

<u>Figure 7</u> and <u>Figure 8</u> give a graphical representation of the model measurement and simulation. The offset line values are given in degrees and millimeters (length for Taconic RF35 and coaxial cable).

Note that the simulation shows a small error at the higher frequencies due to the inaccuracy of the transistor model and broadband matching block.

2-way Doherty amplifier with BLF888A





AN11325#2

4. Bandwidth in UHF

Simulation shows that a bandwidth of this design, with a midband at approximately 650 MHz, is limited to approximately 50 MHz, which is the minimum (40 %) efficiency with a DVB-T signal.



The number of different Doherty combiner designs to cover the whole UHF band can be determined from <u>Figure 10</u>. For example, a fractional bandwidth of 0.07 results in nine different combiner designs, while a fractional bandwidth of 0.11 results in six different combiner designs. A full band design (470 MHz to 860 MHz) would need a fractional bandwidth of approximately 0.6.

AN11325



5. Narrowband designs

5.1 Summary

In total four combiner designs were created and tested:

- 675 MHz
- 710 MHz
- 770 MHz
- 500 MHz

The 675 MHz and 710 MHz designs are similar, only differing in the 90° line.

The combiner lengths are shown in Table 1.

Note that:

• The 500 MHz design is not made on the combiner PCB because of the size of the offset lines (design with coaxial cables)

- The offset line length at 675 MHz is not optimum and this will result in slightly lower efficiency compared to 710 MHz
- The broadband matching of the amplifier blocks has a significant influence on the measured efficiency
- The broadband amplifiers were not correctly tuned below 500 MHz which influenced the result of the 500 MHz design at the lower frequencies
- In some measurements, extra attenuation at the input of the main amplifier was added (parallel 50 Ω resistor to ground). This only gave slightly better results. This was frequency-dependent due to the changing input matching over frequency. A better option would be to use an asymmetrical splitter design.

Table 1.	Combiner	characteristics

f (MHz)	Simulation of	fset line Peaki	ng amp	Peaking amp		Main amp	
	Phase offset line (°)	Length (mm) $\varepsilon_r = 3.5$	Length (mm) ε _r = 2.03 (coax)	Length offset line (mm)	Actual length offset line (mm)	Length offset line +90° (mm)	Actual length offset line +90° (mm)
470	18	19	22.40			115.23	
500	175	177	204.71			267.45	
500				200	200 (coaxial)		300 (coaxial)
550	136	125	144.63			207.23	
600	107	90	104.30			165.38	
650	85	66	76.49			135.58	
665	79	60	69.48			128.01	
675	75	55.8	64.99	55.48		122.80	
675				43	43 (PCB)		117 (PCB)
700	64	46	53.48	46		110.61	
710	59.9	42.4	49.34	42.40		106.10	
710				43	43 (PCB)		102 (PCB)
750	40	27	31.19	27		87.30	
770	29.3	19.1	22.26	19.10		77.84	
770				12	12 (PCB)		69 (PCB)
790	18	11	13.33	11		68.25	
800	12	7.5	8.77	7.5		64.03	
860	159	93	108.14	93		145.59	
870	154	89	103.53	89		140.98	

5.2 Design 1: 675 MHz/710 MHz

Doherty combiner design at 675 MHz and 710 MHz: the designs are similar, only differing in the 90° line.



5.3 Design 2: 770 MHz

Doherty combiner design at 770 MHz:



- Length 90° line = 57 mm
- Length offset line = 12 mm
- Length 35 Ω line = 50 mm
- PCB Taconic; $\varepsilon_r = 3.5$

5.4 Design 3: 500 MHz

Doherty combiner design with coaxial cables. Due to length of the offset line, the PCB is too small.

- Length 90° line = 100 mm
- Length offset line = 200 mm
- Length 35 Ω line = 100 mm
- PCB Taconic; $\varepsilon_r = 2.03$

5.5 DVB-T Measurements: P_{avg} = 200 W, except 770 MHz P_{avg} = 220 W



2-way Doherty amplifier with BLF888A



5.5.1 Supplementary measurement conditions for Figure 14 and Figure 15

- 500 MHz: V_{GS} peaking = 0.75 V; no parallel 50 Ω resistor at input of main amplifier
- 675 MHz: V_{GS} peaking = 0.5 V; parallel 50 Ω resistor at input of main amplifier
- 710 MHz: V_{GS} peaking = 0.9 V; no parallel 50 Ω resistor at input of main amplifier
- 770 MHz: V_{GS} peaking = 0 V; parallel 50 Ω resistor at input of main amplifier.

5.6 Multiple bands

This Doherty design shows multiple bands, this was already seen in simulation.

Multiple bands can also be seen with small signal measurement see (Section 5.6.1).

Whether the multiple bands fall in the UHF band, depends on the total phase shift (output) of amplifier, offset line and 90° line. With 9.90° total phase shift, other bands can be used. In this application the phase shift (mid-band) of the amplifier block plus offset line is 4.90° . The impedance inverter will complete the total phase shift to 5.90° .

Note that in the present designs the multiple bands cannot be used (see Table 2).

- The input splitter has a constant phase shift which is not in line with the output impedance inverter. This will reduce peak power significantly for the other bands (in the target band the phase shift error is small enough not to cause peak power loss).
- Z_{main} in back-off in the multiple bands will not be constant but will increase dependent on frequency. This will cause higher efficiency, giving a η_D of 49.28042 % at 550 MHz (see <u>Table 2</u>). A too high Z_{main} (in back-off) causes a problem with the peak (back-off) voltage because the maximum voltage swing cannot be achieved (knee voltage and/or breakdown limitation). This can result in lower efficiency and worse linearity. Note that this effect is dependent on the total phase shift in the amplifier (thus the increase of Z_{main} is less with e.g. 9.90° than 5.90°, <u>Section 5.6.1</u>.

5.6.1 Simulation for ideal network



2-way Doherty amplifier with BLF888A



 Table 2.
 DVB-T measurement values: 770 MHz Doherty combiner; multiple band at approximately 550 MHz

f (MHz)	V _{DS} (V)	P _i (dB)	P _L (W)	G _p (dB)	Left IMD _{shidr} (dBc)	Right IMD _{shldr} (dBc)	I _{D1}	I _{D2}	η _D (%)	P (W)	CCDF 0.1 %
570	49.35724	-14.6456	198.1	15.17	-19.6103	-19.109	6.11164	4.72278	37.04486	336.6571	6.610577
560	49.44655	-14.4517	198.3	15.47	-21.3721	-20.7245	5.16053	4.0945	43.33201	259.3293	6.442308
550	49.50541	-14.3658	198.6	15.66	-23.2219	-22.2718	4.58328	3.55724	49.28042	204.3998	6.274038
540	49.48266	-13.1682	200.3	15.54	-22.1288	-21.1987	4.92998	3.5018	48.00745	216.9269	6.153846
530	49.37716	-11.6353	198.7	14.94	-22.5852	-20.5922	6.03872	4.27817	39.00524	310.7187	6.298077

2-way Doherty amplifier with BLF888A



AN11325#2

2-way Doherty amplifier with BLF888A



5.7 Thermal considerations

Figure 22 and Figure 23 show thermal properties for a Class AB push-pull amplifier and for a Doherty amplifier with two transistors - one for main, and one for peaking.

It can be seen that although the overall dissipation is less in a Doherty amplifier (40 % compared to e.g. 25 % to 30 %) the thermal stress on the main amplifier can be much greater.

Conditions for the calculation:

- P_{L(AV)} = 120 W average; DVB-T, PAR 8 dB
- R_{th(j-case)} = 0.15 K/W
- T_{case} = 100°C
- Doherty: 85 % dissipation in Main amplifier
- Dissipation +25 % (non-ideal matching)
- Lifetime TTF 0.1 % (failure fraction: p = 0.001)



2-way Doherty amplifier with BLF888A



It can be seen in <u>Figure 23</u> that for a junction temperature of 150 °C in class AB mode, 30 % efficiency is required. In a Doherty amplifier, the efficiency for the same junction temperature is minimum 44 %. The reason is that almost all dissipation (85 %) in Doherty is in the main amplifier in comparison with class AB where dissipation is spread over two transistors.

Note that in a Single Package Doherty (SPD) the thermal stress on the main amplifier improves significantly but this is not covered in this Application Note.

6. Doherty amplifier board

The test circuit (Figure 24 and Figure 25) has been designed on a Taconic RF35 PCB: $h = 0.762 \text{ mm}; \epsilon_r = 3.48.$

Figure 26 shows the combiner designs.

AN11325#2

AN11325



aaa-007210

Fig 24. Demo board for 710 MHz design RF testing

Table 3. Demo board characteristics and operating conditions

Торіс	Parameter	Conditions	Detail
Demo board		output, input and Doherty combiner PCBs	Doh_BLF888A_pcb_V2.dxf
		serial number	NA-1697, NA-xxxx
Supply voltage			50 V
I _{Dq}	quiescent drain current	main amplifier	1.2 A
V _{GS}	gate-source voltage	peaking amplifier; dependent on tested configuration and frequency	0.9 V
Test equipment			
measurement	network analyzer		Rohde & Schwarz ZVR
modeling	ADS		Agilent Advanced Design System
Test signals			
DVB-T		DVB-T signal with shoulder distance	4.3 MHz from $\rm f_{c}$
Pulse		10 % pulsed CW	100 μs

AMPLEON

2-way Doherty amplifier with BLF888A

AN11325



AMPLEON

AN11325 2-way Doherty amplifier with BLF888A



Table 4. List of components

For test circuit PCB layout see Figure 25

Component	Description	Value	Remarks
B1, B2	semi-rigid coax cable	25 Ω, 49.5 mm	UT-090C-25 (EZ 90-25
C1	multilayer ceramic chip capacitor	12 pF	
C2, C3, C4, C5, C6	multilayer ceramic chip capacitor	8.2 pF	
C7	multilayer ceramic chip capacitor	6.8 pF	
C8	multilayer ceramic chip capacitor	2.7 pF	
C9	multilayer ceramic chip capacitor	2.2 pF	
C10, 13, C14	multilayer ceramic chip capacitor	100 pF	
C11, C12	multilayer ceramic chip capacitor	10 pF	
C15, C16	multilayer ceramic chip capacitor	4.7 μF, 50 V	KEMET C1210X475K5RAC-TU or capacitor of same quality
C17, C18, C23, C24	multilayer ceramic chip capacitor	100 pF	
C19, C20	multilayer ceramic chip capacitor	10 μF, 50 V	TDK C570X7R1H106KT00N or capacitor of same quality
C21, C22	electrolytic capacitor	470 μF, 63 V	
C30	multilayer ceramic chip capacitor	10 pF	
C31	multilayer ceramic chip capacitor	9.1 pF	
C32	multilayer ceramic chip capacitor	3.9 pF	
C33, C34, C35	multilayer ceramic chip capacitor	100 pF	
C36, C37	multilayer ceramic chip capacitor	4.7 μF, 50 V	TDK C4532X7R1E475MT020U or capacitor of same quality
L1	microstrip	-	(W \times L) 15 mm \times 13 mm
AN11325#2	All information provided in this docu	ment is subject to legal disclaimers.	© Ampleon The Netherlands B.V. 2015. All rights reserved.

Table 4. List of components ... continued

For test circuit PCB layout see Figure 25

Component	Description	Value	Remarks
L2	microstrip	-	(W \times L) 5 mm \times 26 mm
L3, L32	microstrip	-	(W \times L) 2 mm \times 49.5 mm
L4	microstrip	-	(W \times L) 1.7 mm \times 3.5 mm
L5	microstrip	-	(W \times L) 2 mm \times 9.5 mm
L30	microstrip	-	(W \times L) 15 mm \times 13 mm
L31	microstrip	-	(W \times L) 2 mm \times 11 mm
L33	microstrip	-	(W \times L) 2 mm \times 3 mm
R1, R2	wire resistor	-	
R3, R4	SMD resistor	-	0805
R5, R6	wire resistor	-	
R7, R8	potentiometer	-	

[1] American technical ceramics type 800R or capacitor of same quality

[2] American technical ceramics type 800B or capacitor of same quality

[3] American technical ceramics type 180R or capacitor of same quality

[4] American technical ceramics type 100A or capacitor of same quality

[5] Printed-Circuit Board (PCB): Taconic RF35 ε_r = 3.5 F/m; height = 0.762 mm; Cu (top bottom metallization); thickness copper plating = 35 μ m.

7. Abbreviations

Table 5.	Abbreviations
Acronym	Description
ADS	Advanced Design System
CCDF	Complementary Cumulative Distribution Function
DVB-T	Digital Video Broadcast - Terrestrial
PCB	Printed-Circuit Board
TTF	Time-to-Failure
UHF	Ultra High Frequency

8. Legal information

8.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Ampleon does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

8.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, Ampleon does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Ampleon takes no responsibility for the content in this document if provided by an information source outside of Ampleon.

In no event shall Ampleon be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Ampleon' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of Ampleon.

Right to make changes — Ampleon reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — Ampleon products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Ampleon product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Ampleon and its suppliers accept no liability for inclusion and/or use of Ampleon products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. Ampleon makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Ampleon products, and Ampleon accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Ampleon product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Ampleon does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Ampleon products in order to

avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Ampleon does not accept any liability in this respect.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. Ampleon, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall Ampleon, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of Ampleon, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Translations — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

8.3 Licenses

ICs with DVB-T or DVB-T2 functionality

Use of this product in any manner that complies with the DVB-T or the DVB-T2 standard may require licenses under applicable patents of the DVB-T respectively the DVB-T2 patent portfolio, which license is available from Sisvel S.p.A., Via Sestriere 100, 10060 None (TO), Italy, and under applicable patents of other parties.

8.4 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

Any reference or use of any 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademarks will be replaced by reference to or use of Ampleon's own Any reference or use of any 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademark will be replaced by reference to or use of the 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademarks will be replaced by reference to or use of Ampleon's own trademarks.

9. Contents

1	Introduction	. 3
2	Test circuit	. 3
3	Measurement and modeling	. 4
3.1	Measurement with Network Analyzer	. 4
3.2	Modeling	. 5
3.3	Measurement results	. 7
4	Bandwidth in UHF	. 9
5	Narrowband designs	10
5.1	Summary	10
5.2	Design 1: 675 MHz/710 MHz	12
5.3	Design 2: 770 MHz	13
5.4	Design 3: 500 MHz	14
5.5	DVB-T Measurements: P _{avg} = 200 W, except	
	770 MHz P _{avg} = 220 W	14
5.5.1	Supplementary measurement conditions for	
	Figure 14 and Figure 15	15
5.6	Multiple bands	15
5.6.1	Simulation for ideal network	16
5.7	I hermal considerations	19
6	Doherty amplifier board	21
7	Abbreviations	25
8	Legal information	26
8.1	Definitions	26
8.2	Disclaimers	26
8.3	Licenses	26
8.4	Trademarks	26
9	Contents	27

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© Ampleon The Netherlands B.V. 2015.

All rights reserved.

For more information, please visit: http://www.ampleon.com For sales office addresses, please visit: http://www.ampleon.com/sales

Date of release: 1 September 2015 Document identifier: AN11325#2