

NA-1686

BLF188XR at 41 MHz

Rev. 4 — 05 October 2015

AMPLEON

Application Measurement
Report

Document information

Info	Content
Keywords	NA-1686, 41MHz, BLF188XR
Abstract	Demo board for 41 MHz using BLF188XR

Revision history

Rev	Date	Description
1	20121106	
2	20121204	Update mechanical drawings and dxf files
3	20150424	Update for web publication
4	20151005	The format of this document has been redesigned to comply with the new identity guidelines of Ampleon. Legal texts have been adapted to the new company name where appropriate.

1. Introduction

1.1 General Description

This document shows the measurement results of a 41 MHz push pull demo amplifier (Board NA-1686, with one BLF188XR.)

The demo amplifier can generate over 1200 Watts of pulsed (100uSec, 10%DC) to CW output power at efficiencies of about 82 %.

1.1.1 Test object details

Transistor type: BLF188XR bolted down, using WPS2 compound

Production code:

Package: SOT539A

Board: Output: Coax frafo output circuit 1

Input: Core trafo input circuit 1

On full copper cooling base plate, water channel in base plate

Demo number: NA-1686

2. Design

2.1 Design considerations

The goal was to design a compact circuit for use at 41 MHz using the new BLF188XR LDmosfet. The amplifier should be capable of producing an output power of 1.2 kW and an efficiency of more than 80%. The demo amplifier should be able to survive extreme mismatch conditions as common in laser and plasma generator operation.

To build this design on a standard size base plate of 80 mm * 152 mm the input circuit was designed using a compact 9:1 impedance ferrite transformer. This made it possible to shrink the input circuit size and increase space for the output circuit.

Gate biasing is done via the secondary winding of the input transformer.

The Output circuit was designed using a cable transformer and a cable balun.

No ferrite was used in the output circuit, because of concerns the ferrite might saturate under extreme mismatched load conditions. Drain bias is applied using coils directly to the drain, this makes it possible to dampen drain resonances if necessary.

3. Tests

3.1 Used Test signals

Power/efficiency measurements.

Pulsed, 100uS, Duty Cycle=10% and full CW, Measured at 41MHz.

VSWR testing:

Phase unit capable of VSWR 70 – 90 over 140 degrees of phase angle variation. RG213 cable lengths used to shift the phase angle to cover the whole 360 degrees . This RG224 cable is used to add losses to reach lower VSWR test values. This way the whole 360 degrees could be made with VSWR values from abt 10:1 through 90:1


3.2 Circuit details

The test circuit has been designed on Taconic RF35, h=0.76mm, e r=3.5, 2x35um copper. Supply voltage (drain-source) is typical 50V. To set the drain quiescent current, slowly increase Vg until the total Idq is 100mA.


The demo circuit produces an output power of over 1200 Watts (abt 5dB compressed) , at 82 % efficiency at 41MHz.

4. Measurement Results

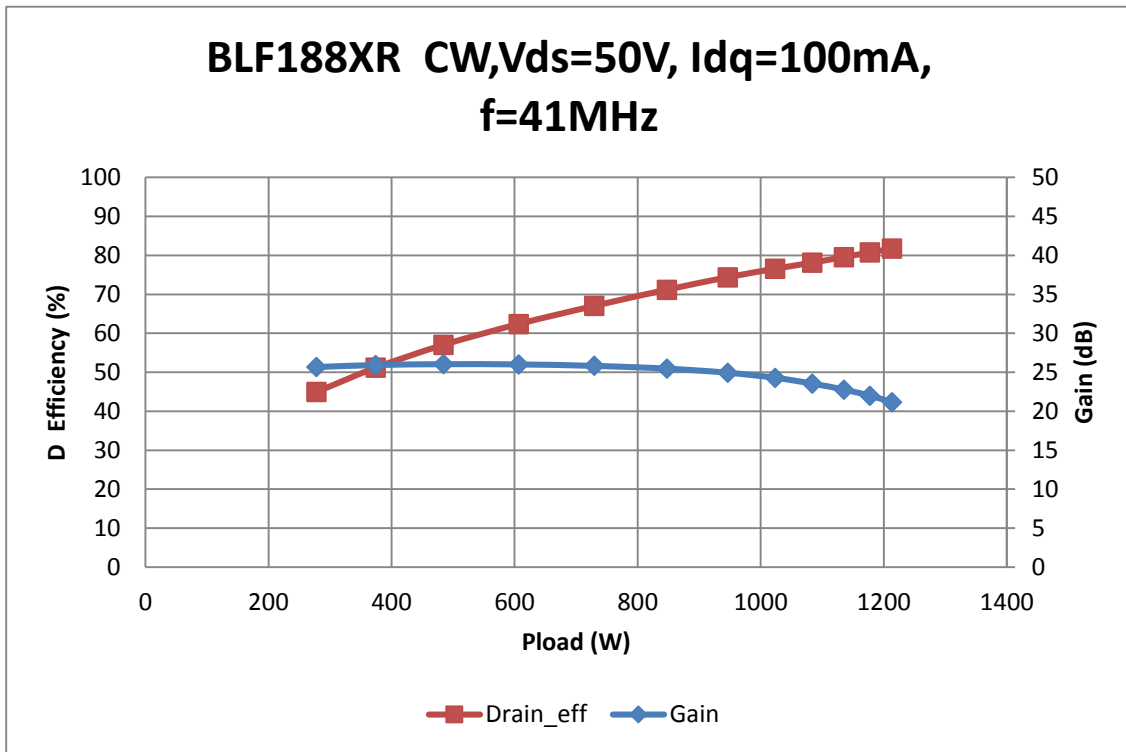4.1 CW/Pulsed – Power Sweep and VSWR testing.



a.

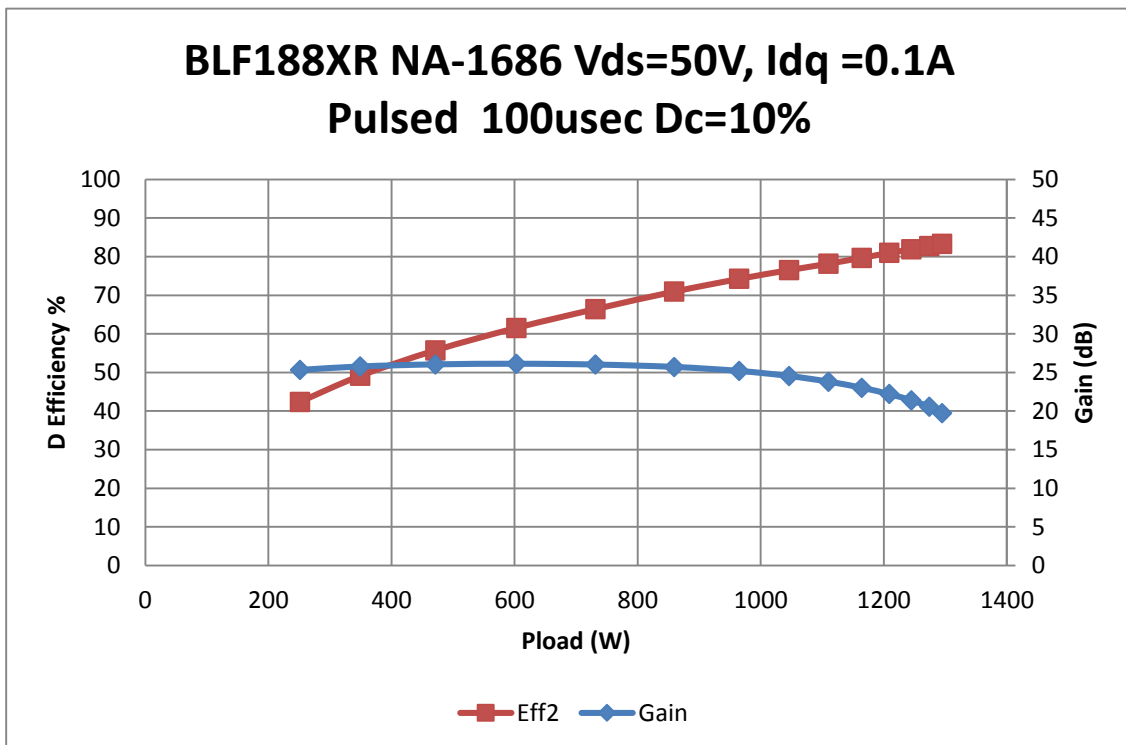


VSWR testing results

VSWR testing NA1686 Pulsed $T_p=100\mu\text{Sec}$, Duty cycle=10% 70MHz mismatch unit used with cables Vswr 10:1 through 90:1 all phases Vds=50 Volts, Idq=200mA complete amplifier						
Pload (W)	10:1	20:1	30:1	60:1	80:1	60-90:1
1000	pass	pass	pass	pass	pass	pass
1100	pass	pass	pass	pass	Pass	pass
1200	pass	pass	pass	pass	pass	pass

5. PCB Layout, Component list

5.1 PCB Layout Drawings

Input circuit, pcb with components

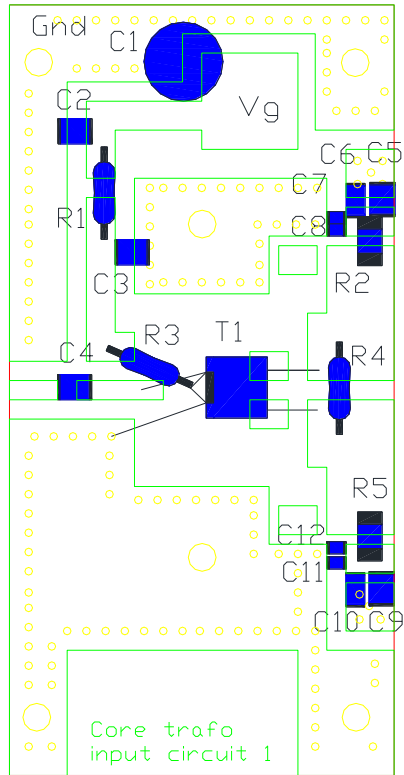


Input circuit, layout with components

5.2 Component list

Components list input circuit.			
C1	220uF	Electrolitic	63V
C2, C3,C4	1nF	ATC100B	
C5,C9	4.7uF	murata	50V
C6,C10	100nF	tdk	
C7,C11	100nF	murata	100V
C8,C12	1nF	ATC700A	
R1,R3	27 Ω	Wired Resistor 0.25W	
R4	2x22Ω	1W wired	Resistors parallel
R2,R5	10Ω	1208 smd	
T1	Two hole core 14x13mm	BM61-202 Material	9:1 transformer P: 1.5wnd isolated wire S: 0.5wnd0.8mm enamel wire
PCB Material: Taconic RF35, Thickness 0,76 mm, εR = 3.5, Cu = 35 micron, double sided copper			



Output circuit, pcb with components

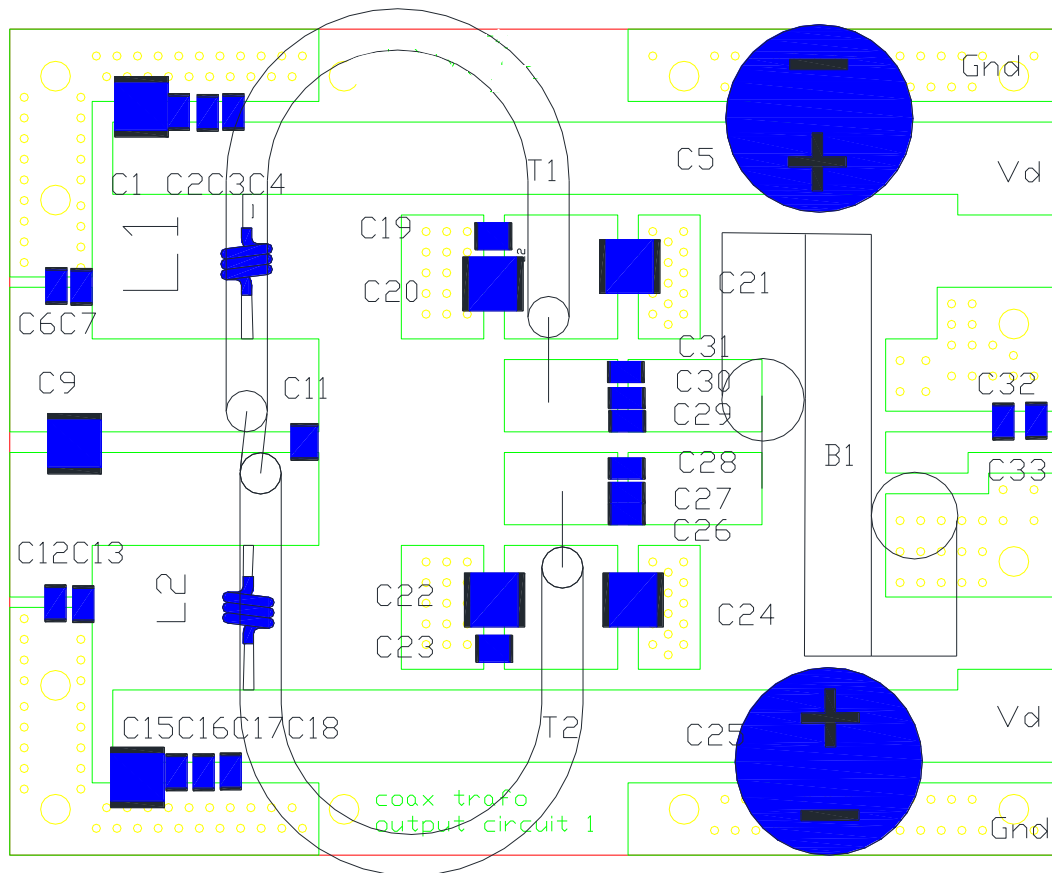


Components Output circuit

Components list output circuit.			
C1,C15	4.7uF	TDK	100V
C2,C16	1nF	ATC800B	
C3,C17	1uF		
C4,C18	220nF		
C5, C25	470uF		
C6, C12	75 pF	ATC800B	
C7, C13	100pF	ATC800B	
C9	36pF	CDE min300V	
C11	24pF	ATC800B	
C20,21,22,24	4.7uF	TDK	100V
C19,23	1nF	ATC100B	
C26 –C31	1nF	ATC100B on side	
C32	33pF	ATC800B	
C33	43pF	ATC800B	
L1,2	4turns 6mm inner diameter	1.5mm enamel wire	Close wound
T1,T2	Coax 12Ohms	Sucoform_F L=300mm	Wound up to make 1.5 winding
B1	50 ohms one line	RG142 L=500mm	Wound up to make 3windings.
PCB Material: Taconic RF35, Thickness 0,76 mm, εR = 3.5, Cu = 35 micron, double sided copper			


5.3 Photos of Demo Board

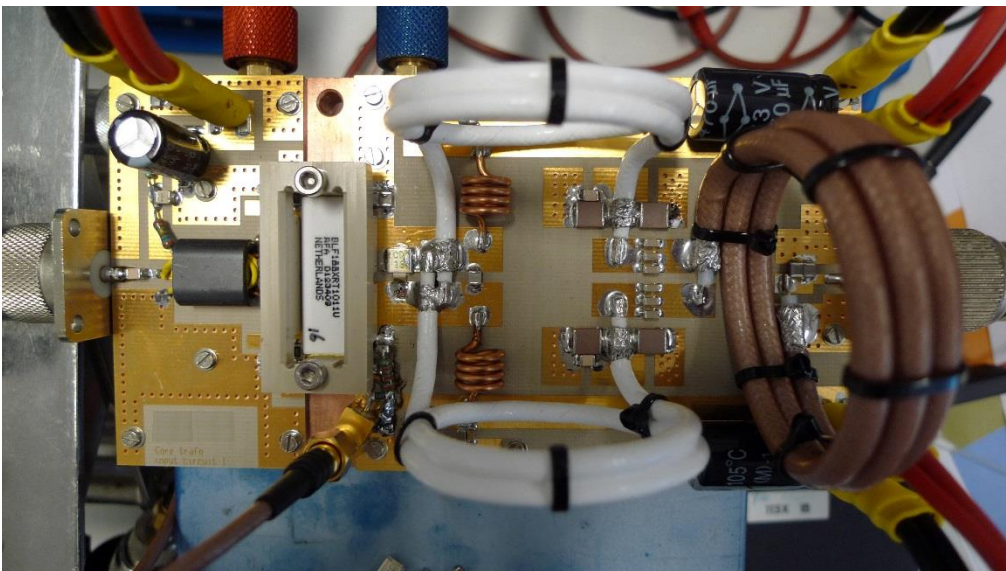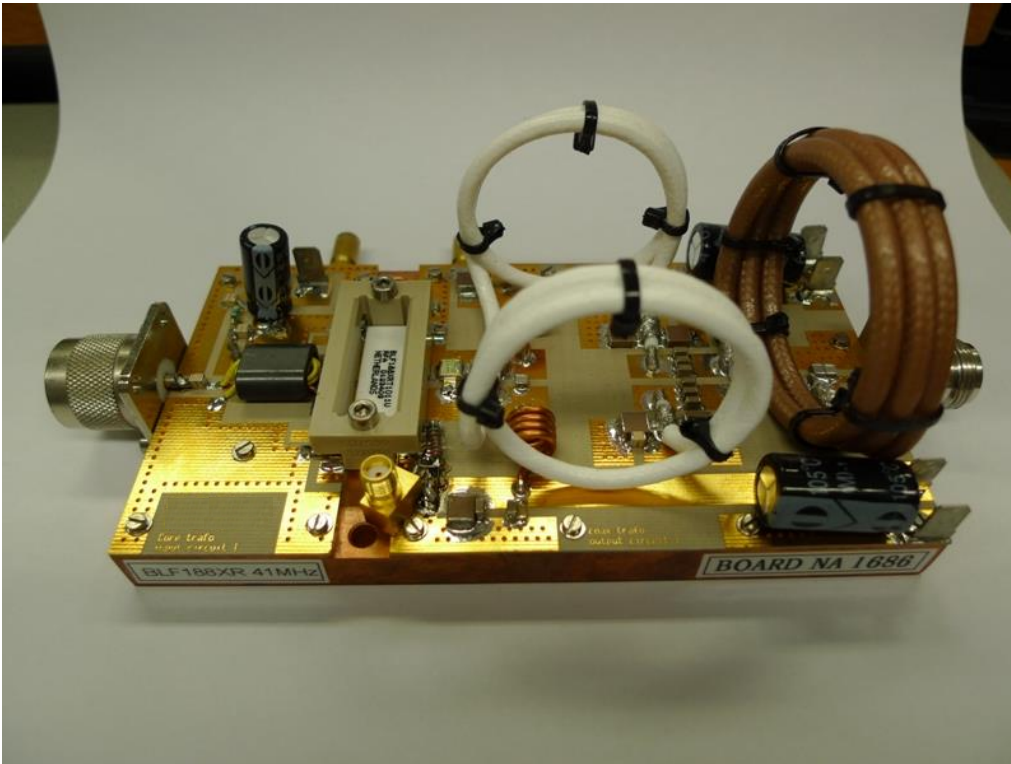

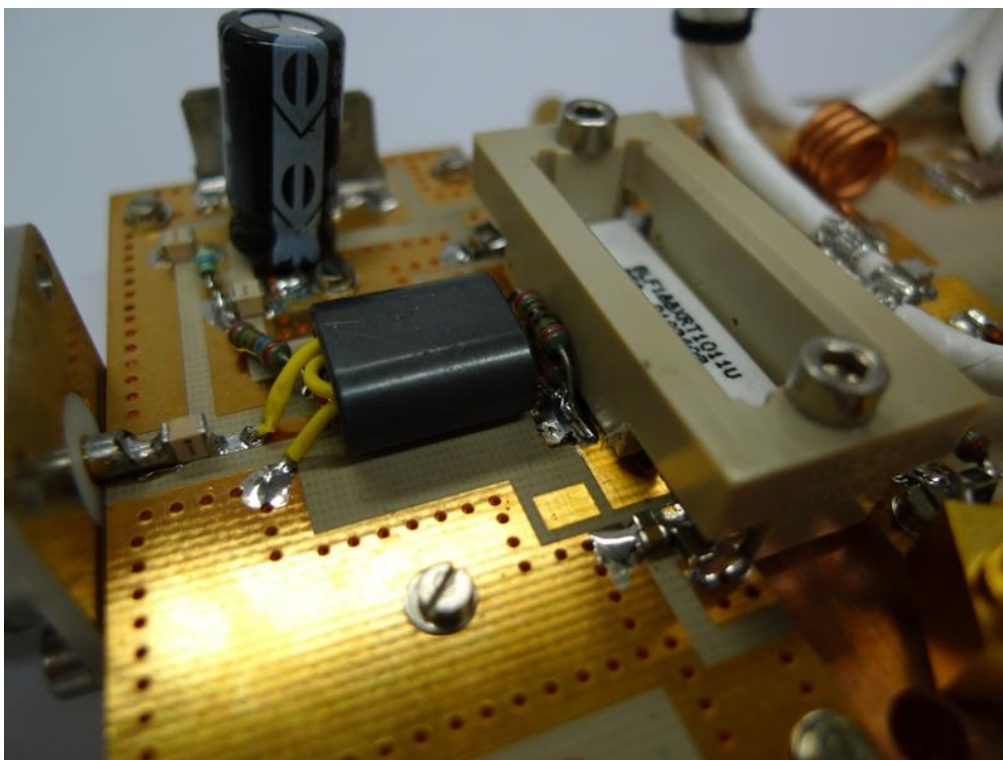

Detail of input matching circuit, 9:1 transformer construction.

5.4 Base plate mechanical drawings

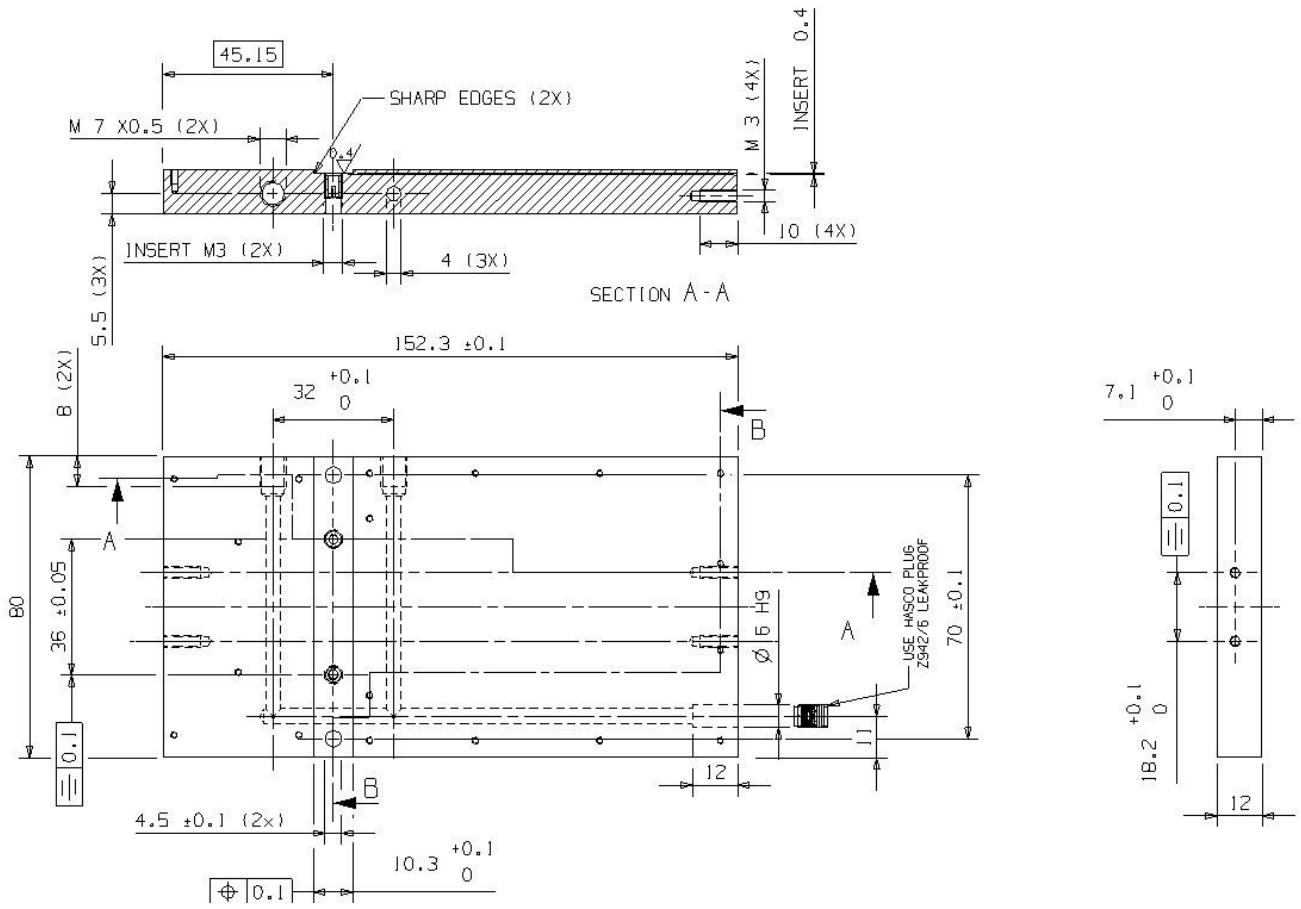

6. Attachments

Please see the attachment for the support files.

7. Legal information

7.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Ampleon does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

7.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, Ampleon does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Ampleon takes no responsibility for the content in this document if provided by an information source outside of Ampleon.

In no event shall Ampleon be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Ampleon's aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of Ampleon.

Right to make changes — Ampleon reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — Ampleon products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Ampleon product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Ampleon and its suppliers accepts no liability for inclusion and/or use of Ampleon products in

such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. Ampleon makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Ampleon products, and Ampleon accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Ampleon product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Ampleon does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Ampleon products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Ampleon does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

7.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

Any reference or use of any 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademarks will be replaced by reference to or use of Ampleon's own trademarks.

7.4 Contact information

For more information, please visit: <http://www.ampleon.com>

For sales office addresses, please visit: <http://www.ampleon.com/sales>

8. Contents

1.	Introduction	3
1.1	General Description	3
1.1.1	Test object details	3
2.	Design	3
2.1	Design considerations	3
3.	Tests	4
3.1	Used Test signals	4
3.2	Circuit details	4
4.	Measurement Results	5
4.1	CW/Pulsed – Power Sweep and VSWR testing	5
5.	PCB Layout, Component list	7
5.1	PCB Layout Drawings	7
5.2	Component list	7
5.3	Photos of Demo Board	10
5.4	Base plate mechanical drawings	12
6.	Attachments	12
7.	Legal information	13
7.1	Definitions	13
7.2	Disclaimers	13
7.3	Trademarks	13
7.4	Contact information	13
8.	Contents	14

Please be aware that important notices concerning this document and the product(s) described herein, have been included in the section 'Legal information'.

© Ampleon B.V. 2015.

All rights reserved.

For more information, please visit: <http://www.ampleon.com>
For sales office addresses, please visit: <http://www.ampleon.com/sales>

Date of release: 05 October 2015
Document identifier: NA-1686