

CD-101-14

BLF881 at 88-108 MHz

Rev. 3 — 05 October 2015

AMPLEON

Application Measurement
Report

Document information

| Info | Content |
|----------|-----------------------------------------------------------------------------------------------------------------------------|
| Keywords | BLF881, FM, 140W CW |
| Abstract | This test report describes an amplifier that outputs more than 140 W from 88 to 108 MHz, using the BLF881 LDMOS transistor. |

Revision history

| Rev | Date | Description |
|------------|-------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 1 | 20140120 | Initial version |
| 2 | 20150424 | Update for web publication |
| 3 | 20151005 | The format of this document has been redesigned to comply with the new identity guidelines of Ampleon. Legal texts have been adapted to the new company name where appropriate. |

1. Introduction

This report describes a FM amplifier based on Ampleon’s BLF881, which works from 88 to 108 MHz, outputs more than 140 W CW power, with very good 2nd and 3rd harmonics.

1.1 Summary

The RF performance can be summarised as follows:

| | |
|---------------------------|--------------------|
| Specified frequency range | 88 to 108 MHz |
| Drain voltage | 50 V |
| Quiescent drain current | 100 mA typ |
| CW power capability | ≥ 140 W(88-108MHz) |
| 2 nd harmonics | <-39dBc |
| 3 rd harmonics | <-53.5dBc |

Table 1. Summary of RF performance

2. RF performance

2.1 Return loss Sweep

The plot below shows return loss as a function of frequency. The network analyzer is using a swept CW signal at 0dBm of input power.

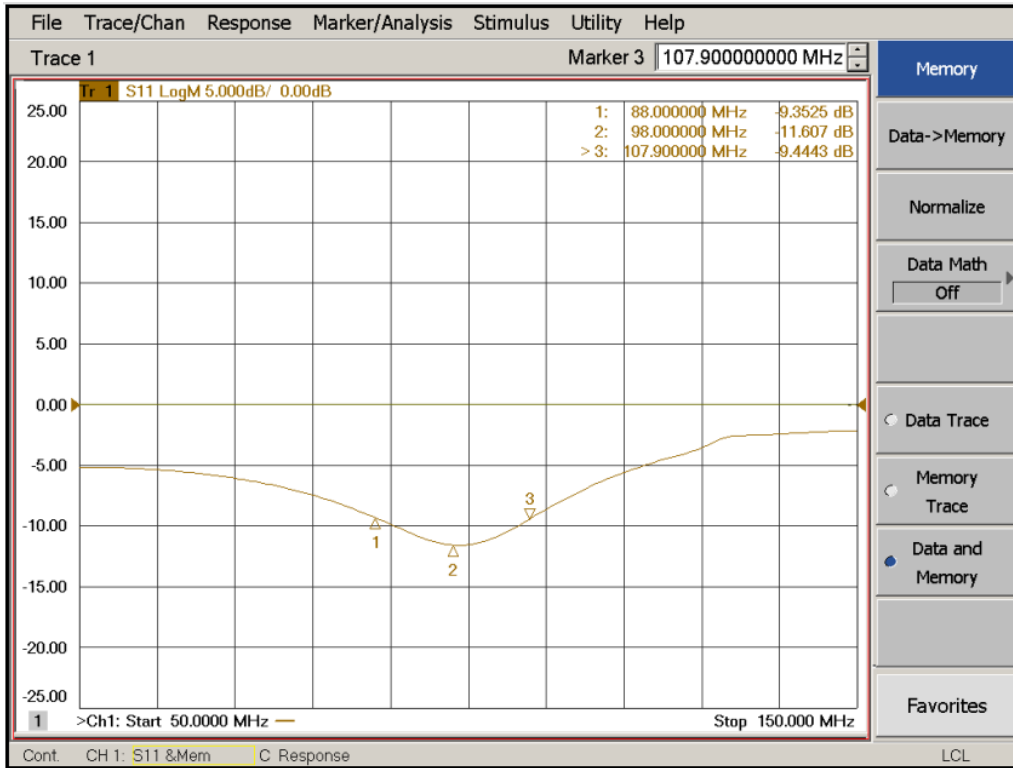


Fig 1. Return loss as a function of frequency

2.2 Gain Sweep

The plot below shows small signal gain as a function of frequency. The network analyzer is using a swept CW signal at 0dBm of input power. The bias is 50V, 350mA.

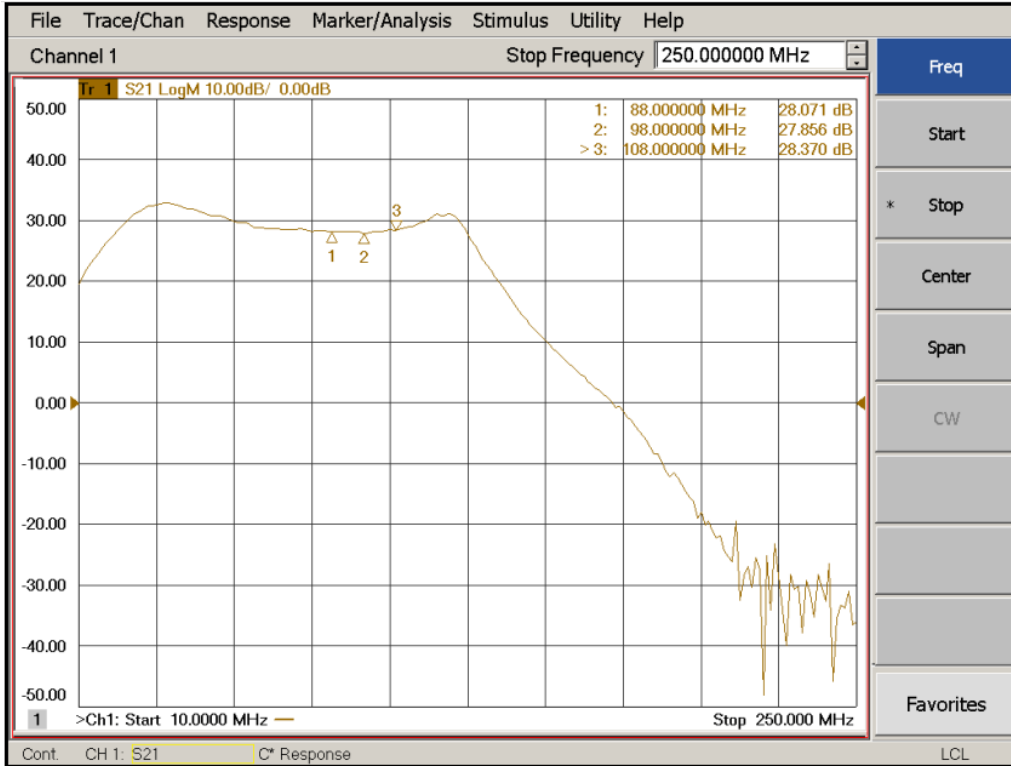


Fig 2. Small signal Gain as a function of frequency

2.3 CW Gain as a Function of Output Power

The plot below shows gain as a function of output power. The bias point is 50V and 100mA. The signal is a CW signal at 88MHz, 98MHz, 108MHz.

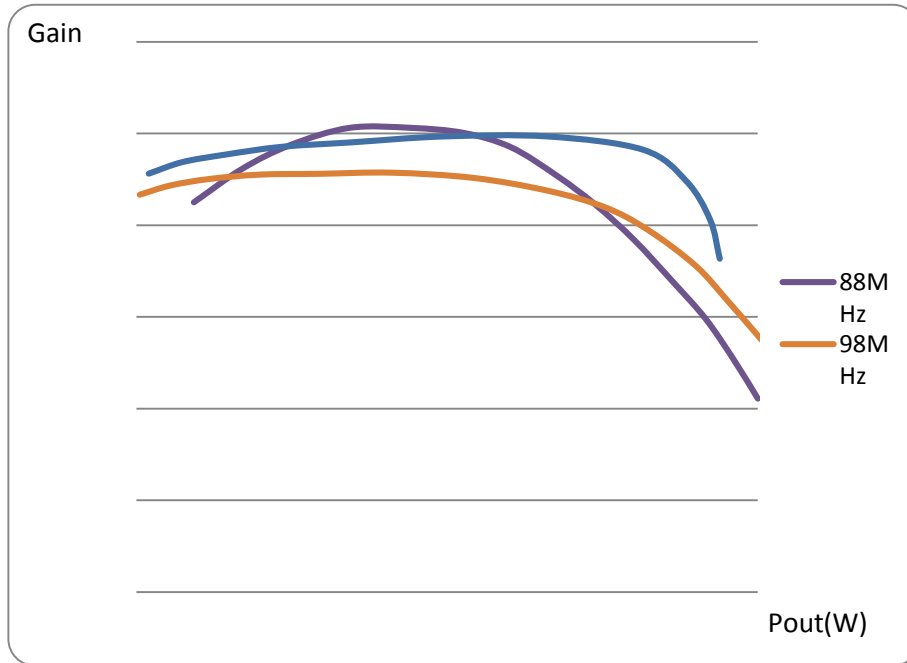


Fig 3. CW gain as a function of output power 88-108MHz

2.4 CW Efficiency as a Function of Output Power

The plot below shows efficiency as a function of output power. The bias point is 50V and 100mA. The signal is a CW signal at 88MHz, 98MHz, 108MHz.

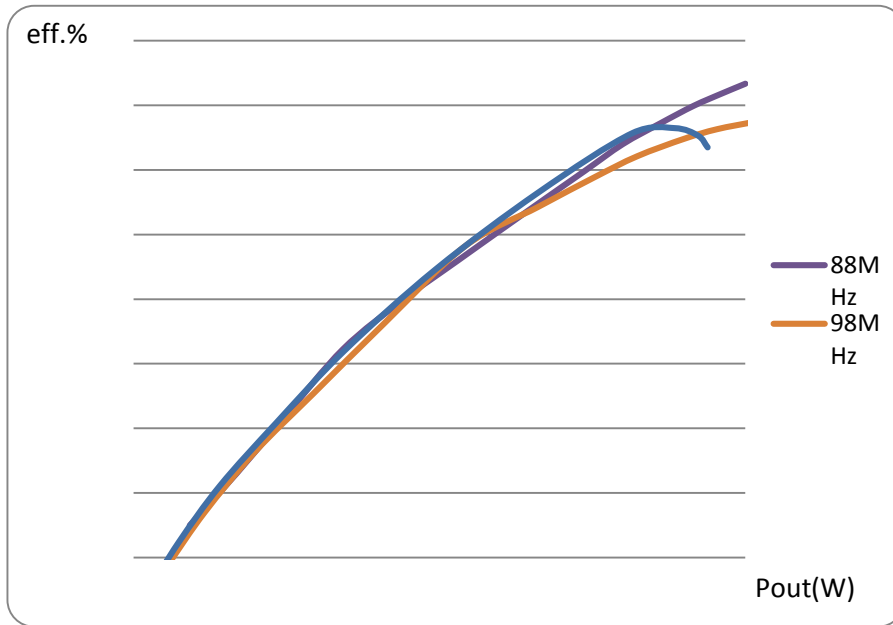


Fig 4. CW efficiency as a function of output power 88-108MHz

2.5 Harmonics

The plot below shows harmonics while the device output power is fixed at 140W CW, and the frequency is swept from 88-108MHz. Max hold is being used on the spectrum analyzer to catch the peak of all the signals. The spectrum is monitored through the circuit, and after the 50 ohm load.

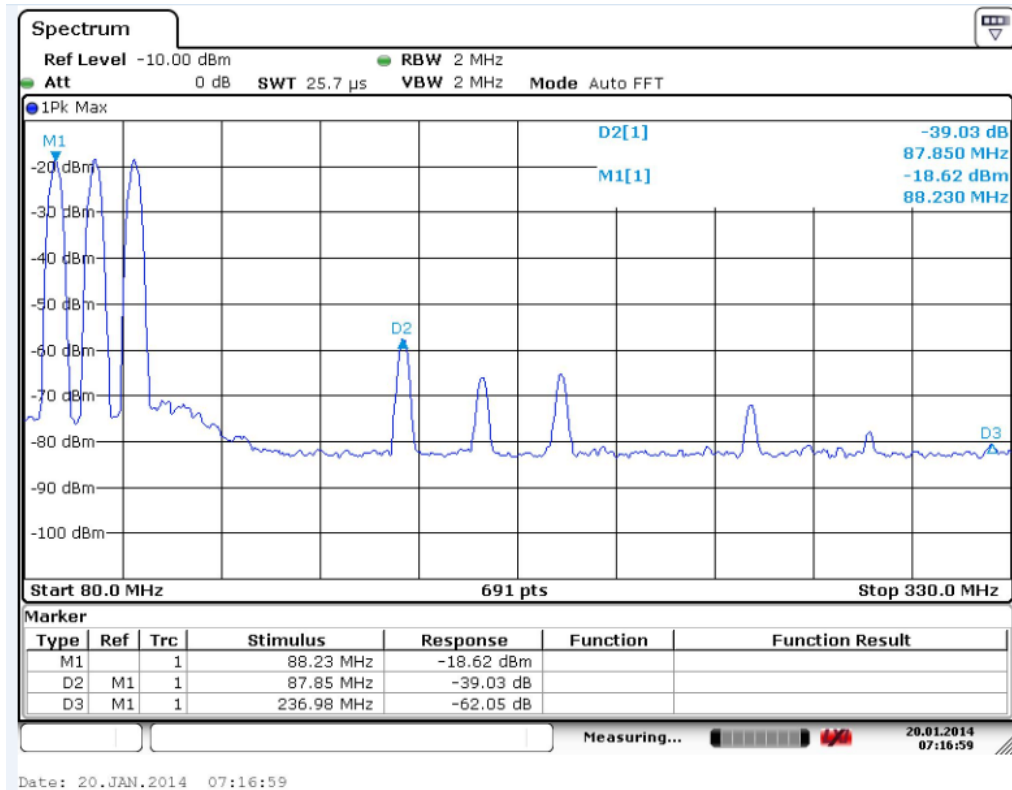


Fig 5. Harmonics at 140W CW 88-108MHz

3. Circuits information

The PCB layout drawing is attached to this report, please find it in the attachment button.


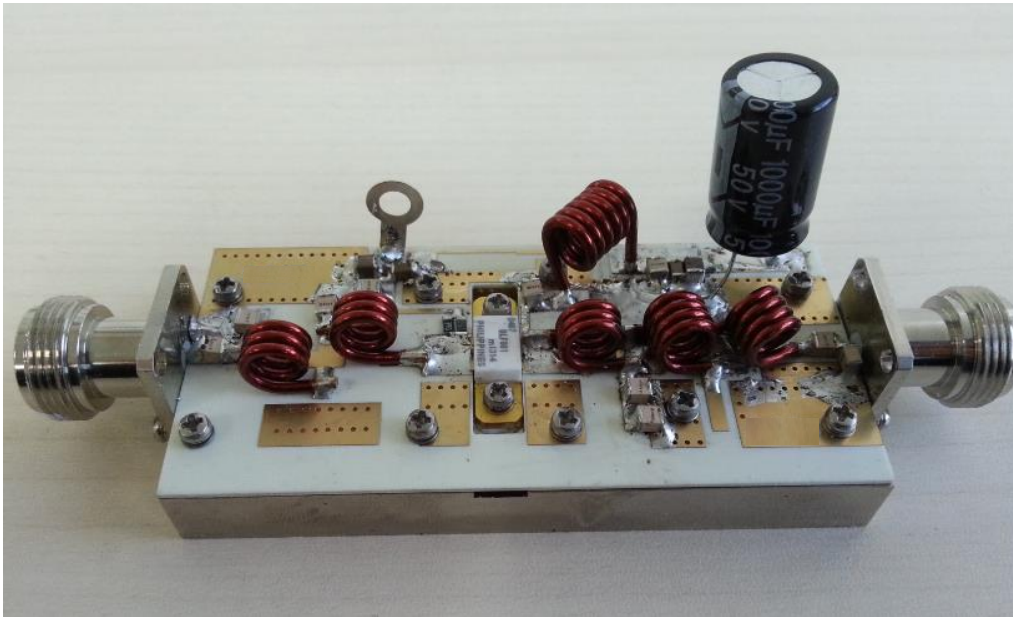


Fig 6. BLF881 88-108 MHz 140W amplifier

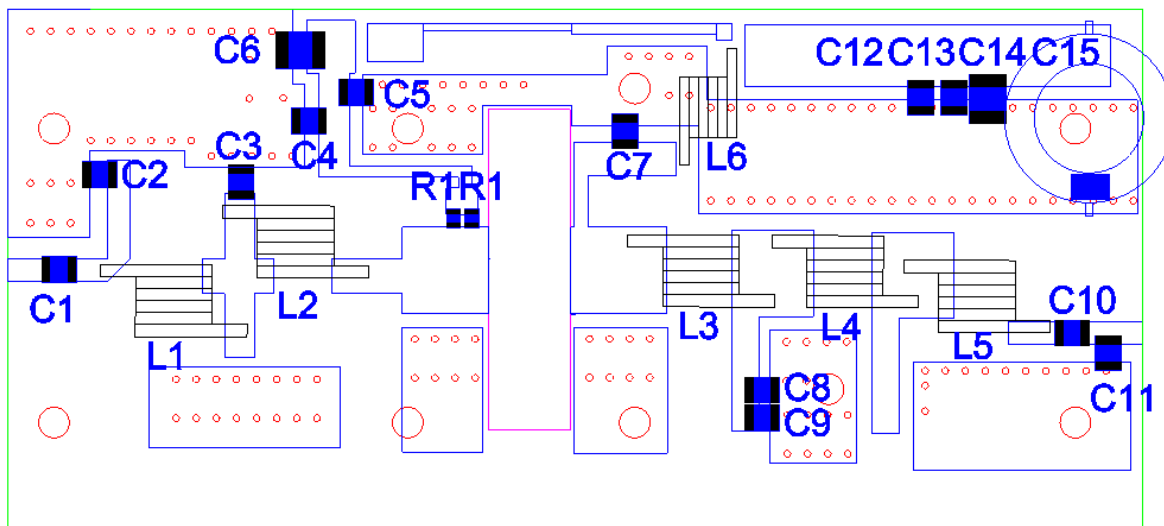

(1) PCB is Rogers Ro4350B; $\epsilon_r = 3.5$; height = 30mil; Cu thickness = 35 μm

Fig 7. PCB layout

Table 2. Bill of materials

| Quantity | Description | Part Number | Manufacturer |
|---------------|-----------------------------------------|----------------------|--------------|
| R1 | 39ohm 0805 Resistor leaded | | |
| R2 | 75ohm 0805 Resistor leaded | | |
| C1,C4,C10,C12 | 1000P | 100B | |
| C2 | 30P | 100B | ATC |
| C3,C7 | 56P | 100B | ATC |
| C8 | 75P | 100B | ATC |
| C9 | 6.8P | 100B | ATC |
| C11 | 24P | 100B | ATC |
| C5,C13 | 0.1uF 50V Ceramic Capacitor | | Kemet |
| C6,C14 | 10uF 50V Ceramic Capacitor | | Kemet |
| C15 | 470 uF 63V Electrolytic Capacitor | MCRH63V477M13 X26-RH | MULTICOMP |
| L1,L2,L3 | Handwound 3 turn 5mm diameter with15AWG | | Handwound |
| L4,L5 | Handwound 4 turn 5mm diameter with15AWG | | Handwound |
| L6 | Handwound 6 turn 5mm diameter with15AWG | | Handwound |
| PCB | Er=3.5, 30mil, 1OZ | RO4350B | ROGERS |

4. Legal information

4.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Ampleon does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

4.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, Ampleon does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Ampleon takes no responsibility for the content in this document if provided by an information source outside of Ampleon.

In no event shall Ampleon be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Ampleon's aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of Ampleon.

Right to make changes — Ampleon reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — Ampleon products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Ampleon product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Ampleon and its suppliers accepts no liability for inclusion and/or use of Ampleon products in

such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. Ampleon makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Ampleon products, and Ampleon accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Ampleon product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Ampleon does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Ampleon products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Ampleon does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

4.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

Any reference or use of any 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademarks will be replaced by reference to or use of Ampleon's own trademarks.

4.4 Contact information

For more information, please visit: <http://www.ampleon.com>

For sales office addresses, please visit: <http://www.ampleon.com/sales>

5. Contents

1. Introduction 3
 1.1 Summary..... 3
 2. RF performance 4
 2.1 Return loss Sweep 4
 2.2 Gain Sweep..... 5
 2.3 CW Gain as a Function of Output Power 6
 2.4 CW Efficiency as a Function of Output Power..... 7
 2.5 Harmonics 8
 3. Circuits information 9
 4. Legal information 11
 4.1 Definitions 11
 4.2 Disclaimers..... 11
 4.3 Trademarks 11
 4.4 Contact information 11
 5. Contents..... 12

Please be aware that important notices concerning this document and the product(s) described herein, have been included in the section 'Legal information'.

© Ampleon B.V. 2015.

All rights reserved.

For more information, please visit: <http://www.ampleon.com>
 For sales office addresses, please visit: <http://www.ampleon.com/sales>

Date of release: 05 October 2015
 Document identifier: CD-101-14